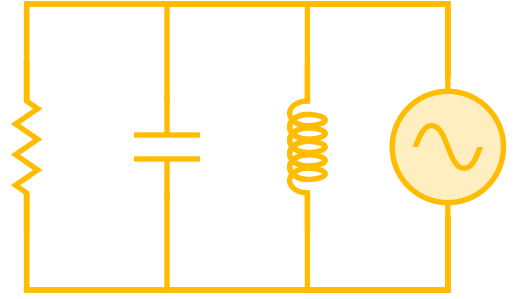


Electric Circuits



→ Rules : AC circuits

instantaneous voltage: $v(t) = V_{max} \sin(\omega t + \theta_v) = V_{rms} \angle \theta_v = \frac{V_{max}}{\sqrt{2}} \angle \theta_v$

instantaneous current: $i(t) = I_{max} \sin(\omega t + \theta_i) = I_{rms} \angle \theta_i = \frac{I_{max}}{\sqrt{2}} \angle \theta_i$

impedance

reactance

phase shift

$$Z = \frac{v(t)}{i(t)} = R + Xj = R + (X_L - X_C)j = |Z| \angle \hat{Z} = |Z| \angle (\theta_v - \theta_i)$$

Resistor

$$Z = R$$

$$X = 0$$



zero reactance

Inductor

$$Z = j\omega L$$

$$X_L = \omega L$$



inductive reactance

Capacitor

$$Z = \frac{1}{j\omega C}$$

$$X_C = \frac{1}{\omega C}$$



capacitive reactance

Power Calculations

instantaneous power:

$$p = vi = V_{max} I_{max} \sin(\omega t + \theta_v) \sin(\omega t + \theta_i)$$

active power:

$$P = V_{rms} I_{rms} \cos(\hat{Z})$$

reactive power:

$$Q = V_{rms} I_{rms} \sin(\hat{Z})$$

apparent power:

$$|S| = V_{rms} I_{rms}$$

complex power: $S = P + Qj$

power factor:

$$P.F. = \cos(\hat{Z}) = \frac{P}{|S|}$$

